

Concordia University
Department of Electrical and Computer Engineering
COEN 316 Computer Architecture
Lab 4 Part 2: Datapath/Control Unit Integration and system testing
Winter 2023

Introduction

The datapath designed in the previous part of this lab contains 10 control signals. The function of the control unit, which is the focus of this part, is to produce the correct values for all the control signals at the proper point in time. Tables 1 and 2 lists the 10 control signals and summarizes their operation.

Table 1: Single bit control signals.

Control signal	value = 0	value = 1
reg_write	do not write into register file	write into register file
reg_dst	rt is the destination register	rd is the destination register
reg_in_src	d_out of data_cache is the d_in to the register file	ALU output is the d_in to the register file
alu_src	out_b of register file (rt) is the y input of the ALU	sign extended immediate is the y input of the ALU
add_sub	ALU operation = addition	ALU operation = subtraction
data_write	do not write into data cache	write into data cache

Table 2: Two bit control signals.

Control signal	value = 00	value = 01	value = 10	value = 11
logic_func	AND	OR	XOR	NOR
func	load upper immediate	set less	arithmetic	logic
branch_type	no branch	beq	bne	bltz

Table 2: Two bit control signals.

Control signal	value = 00	value = 01	value = 10	value = 11
pc_sel	no jump (PC+1, or PC+target address if branch condition is true)	jump (PC = target address)	jump register (PC = rs)	not used

Table 3 lists the 20 instructions implemented by the CPU together with the values of the 6 bit opcode field and the 6 bit func field (contained within the instruction as per Figure 1 of Lab 4) together with the 10 control signals. Table 3 is **partially** completed, you are to **complete** the table by deriving the values of the 10 control signals based upon Tables 1 and 2 and knowledge of which control signals need to be activated during a particular instruction in order to achieve correct execution of the instruction. Refer to your datapath of Part 1 to assist in completing the table.

Table 3: 20 instructions with opcode and function fields and control signals. [1]

Inst.	op	func	reg_wrtite	reg_dst	reg_in_src	alu_src	add_su b	data_w rite	logic_f unc	func	branch _type	pc_sel
lui	001111		1	0	1	1	0 (don't care)	0	00 (don't care)	00	00	00
add	000000	100000	1	1	1	0	0	0	00	10	00	00
sub	000000	100010										
slt	000000	101010										
addi	001000		1	0	1	1	0	0	00	10	00	00
slti	001010											
and	000000	100100	1	1	1	0	1	0	00	11	00	00
or	000000	100101										
xor	000000	100110										
nor	000000	100111										
andi	001100											
ori	001101											
xori	001110											
lw	100011		1	0	0	1	0	0	10 (don't care)	10	00	00

Table 3: 20 instructions with opcode and function fields and control signals. [1]

Inst.	op	func	reg_wri te	reg_dst	reg_in _src	alu_src	add_su b	data_w rite	logic_f unc	func	branch _type	pc_sel
sw	101011											
j	000010											
jr	000000	001000										
bltz	000001											
beq	000100		0	0	0	0	0	0	00	00	01	00
bne	000101											

Note that Table 3 has some entries which are “don’t care” values which have arbitrarily assigned with values.

Procedure

Complete Table 3 by deriving all the remaining values of the control signals. Design the control unit using VHDL. The control unit in this implementation is a combinational logic circuit whose inputs are the opcode and function fields of the instruction and the outputs are the 10 control signals. Test your control unit (through simulation) to ensure that it generates the correct values for the 10 control signal for each of the 20 instructions. You may either use a VHDL process for the control unit which will be added to your datapath designed in Part 1, or you may design the control unit as a separate entity and use it as an additional component to be added with a port map statement to your existing datapath. Alternatively, the datapath of Lab 4 may be added as a component together with an instance of your control unit to create a new top level entity (with name cpu).

Use the following VHDL entity specification for the final CPU design:

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_signed.all;

entity cpu is
port(reset : in std_logic;
      clk   : in std_logic;
      rs_out, rt_out : out std_logic_vector(3 downto 0);

      -- output ports from register file

      pc_out : out std_logic_vector(3 downto 0); -- pc reg
      overflow, zero : out std_logic);
end cpu;
```

You will note that in the cpu entity, the top-level ports consist of the out_a (rs) and out_b (rt) ports of the register file and the PC register. As was done in previous labs, only the low-order 4 bits of these registers shall be constrained to LEDs on the Nexys A7 FPGA board. The overflow and zero output ports will be constrained to available LEDs. There is an asynchronous reset (which will be constrained to a switch input) and a clock input (constrained to a switch on the FPGA board). You may make use of the provided lab4.xdc file. **It is important that you use the above entity specification, as it is the one which will be used during the lab quiz.**

Test your complete CPU by writing different test programs into the I-cache and **verify correct operation of your CPU through simulation. Explain your test programs.**

Questions:

1. In order to demonstrate an awareness of the limitation of tools and hardware (i.e. an FPGA device), examine the FPGA resource utilization report found in the file:

```
project_name/project_name.runs/impl_1/toplevel_entity_name_utilization_placed.rpt
```

to determine the amount of FPGA resources used by your implementation of the entire CPU. In particular, determine the amount of **Slice Logic**, **Registers**, and **SLICEL** and **SLICEM** used. These values will be found in several tables within the report. For example:

1. Slice Logic

Site Type	Used	Fixed	Available	Util%
Slice LUTs	559	0	63400	0.88
LUT as Logic	559	0	63400	0.88
LUT as Memory	0	0	19000	0.00
Slice Registers	1157	0	126800	0.91
Register as Flip Flop	1157	0	126800	0.91
Register as Latch	0	0	126800	0.00

2. Slice Logic Distribution

Site Type	Used	Fixed	Available	Util%
Slice	442	0	15850	2.79
SLICEL	281	0		
SLICEM	161	0		
LUT as Logic	559	0	63400	0.88
using O5 output only	0			
using O6 output only	540			
using O5 and O6	19			

Note: Your actual values may be different depending upon your design of the CPU.

Based upon these values, comment on whether it would be possible to implement on the FPGA device used in the labs, a design consisting of 5, 10, 20, 100 CPUs? For the purposes of this question, it is only necessary to consider the instance of the CPU, we will **not** consider any sort of interconnection network used to communicate between the CPUs. In order to obtain meaningful answers, you are to implement several designs (1 CPU, 5 CPUs, 10 CPUs and tabulate the data and extrapolate from these values. The VHDL port map statement is a convenient method to create a design consisting of multiple instances of your CPU. It will **also be necessary** to set a DONT_TOUCH VHDL **synthesis attribute** on the instantiated instances of the CPU components to prevent the logic synthesis tool from removing them during the optimization phase. To set a DONT_TOUCH attribute on a component instance, one first must declare and assign a value to the attribute. The VHDL syntax is:

```
attribute DONT_TOUCH : string;
attribute DONT_TOUCH of U0 : label is "TRUE";
```

The DONT_TOUCH attribute can either have value of “TRUE” or “FALSE”. In the above, U0 corresponds to the component instance name. One can next create a top-level entity which consists of a specific number of CPUs instantiated as component instances with several port map statements:

```
entity two_cpu is
port(reset : in std_logic;
      clk   : in std_logic); -- intentional that there are no
end two_cpu;                -- output ports (for simplicity)

architecture rtl of two_cpu is

component cpu is
port(reset : in std_logic;
      clk   : in std_logic;
      rs_out, rt_out : out std_logic_vector(3 downto 0);
      pc_out : out std_logic_vector(3 downto 0);
      overflow, zero : out std_logic);
end component ;

-- declare internal signals used in the component
-- port map statements

signal rs_out0, rs_out1 : std_logic_vector(3 downto 0);
signal rt_out0, rt_out1 : std_logic_vector(3 downto 0) ;
signal pc_out0, pc_out1 : std_logic_vector(3 downto 0) ;
signal overflow0, overflow1 : std_logic;
signal zero0, zero1 : std_logic;

for MICK, KEITH : cpu use entity WORK.cpu(rtl);
```

```

attribute DONT_TOUCH : string;
attribute DONT_TOUCH of MICK : label is "TRUE";
attribute DONT_TOUCH of KEITH : label is "TRUE";

-- the DONT_TOUCH attribute is needed for all the instances
-- of the 'cpu' component, otherwise during implementation the
-- optimizer does some "decloning" of all into a single instance
-- and the implemented design consists of only 1 CPU with the
-- resource utilization the same as that of just the
-- original single CPU design

begin

-- component instantiation

MICK: cpu port map(reset => reset, clk => clk, rs_out => rs_out0,
rt_out => rt_out0, pc_out => pc_out0, overflow => overflow0, zero
=> zero0);

KEITH: cpu port map(reset => reset, clk => clk, rs_out => rs_out1,
rt_out => rt_out1, pc_out => pc_out1, overflow => overflow1, zero
=> zero1);

end rtl;

```

One may use a similar approach to design an entity with 5, 10, or more CPUs. It should be noted that within the top-level entity `two_cpu`, there are no output ports. This was intentionally done to simplify the design. Note how the internal signals are simply left “dangling”. Alternatively, one may leave include the output ports within the `two_cpu` entity, and then simply logically OR the internal signals with the output of each OR gate driving the designated output port. For example,

```

rs_out <= rs_out0 or rs_out1;
rt_out <= rt_out0 or rt_out1 ;
pc_out <= pc_out0 or pc_out1;
overflow <= overflow0 or overflow1;
zero <= zero0 or zero1;

```

However, this will cause additional hardware to be created, thus it is easier to simply have no output ports (and the `DONT_TOUCH` attribute will preserve the instantiated instances).

2. Can you think of any other limitations when synthesizing a design with a software logic synthesis tool?

Hint: What resources does software require when executing on a computer?

Hint Hint: Einstein’s Theory of Relativity provided new insight into the nature of space and *time*.

